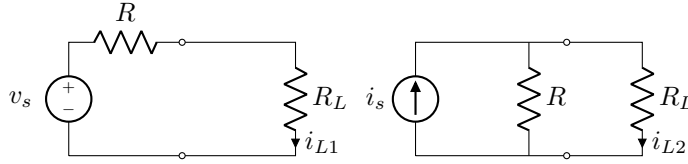


# Lecture 16, Feb 16, 2022

## Source Transformation

- This method is not as strong as nodal analysis or mesh analysis, but gives insight into circuit analysis
- Consider 2 circuits:




- For circuit 1,  $i_{L1} = \frac{v_s}{R + R_L}$  by Ohm's law


\* For circuit 2,  $i_{L2} = i_s \frac{R}{R + R_L}$  by current division

\* If both circuits are equivalent, then we'll get  $i_{L1} = i_{L2} \implies \frac{v_s}{R + R_L} = i_s \frac{R}{R + R_L} \implies v_s = i_s R$

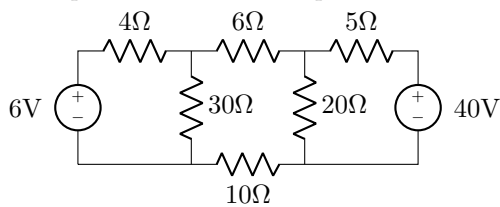
- Source transformation: We can transform a voltage source with a resistor in series to a current source with a resistor in parallel if  $v_s = Ri_s$ 
  - The direction of the sources do not follow PSC
- Example circuit: Find the power of the 6V source:



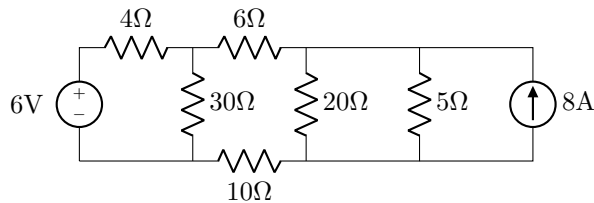
- Convert voltage source with series resistor to current source with parallel resistor:



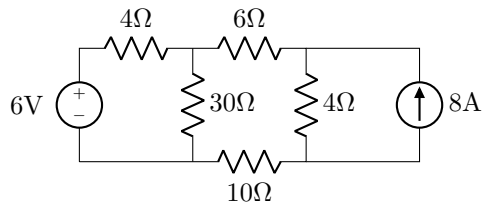
- Now we can simplify the two resistors in parallel on the right side:



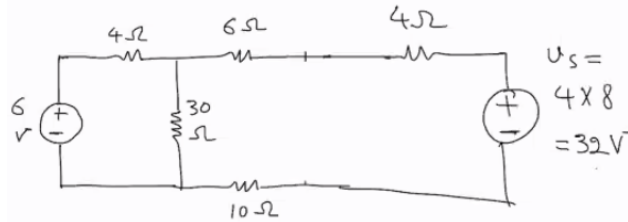
- Now transform the current source and parallel resistor to a voltage source and a series resistor:




- Simplify series resistors:

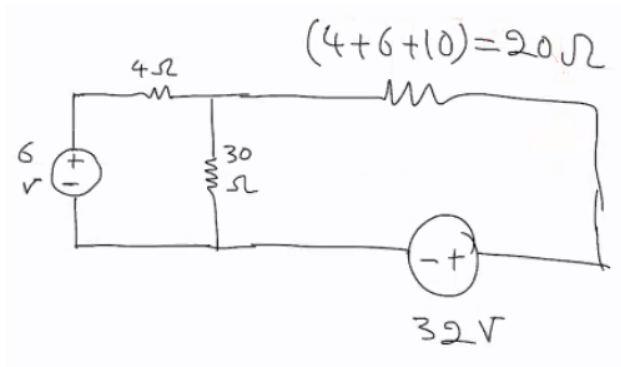

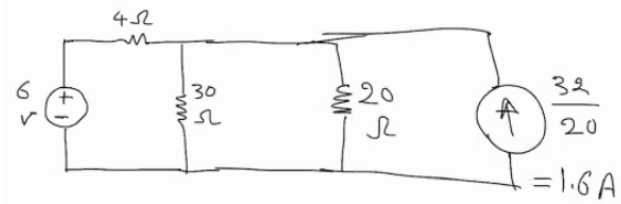
- Convert voltage source to current source:




- Simplify parallel resistors:

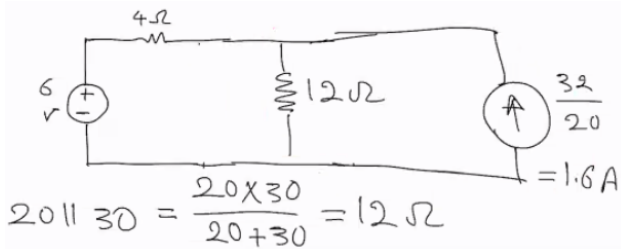

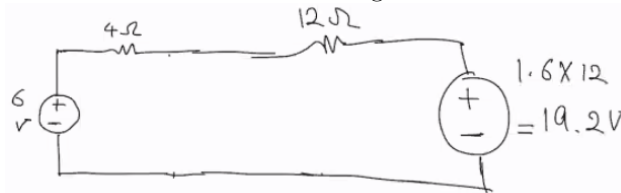- Convert current source to voltage source:



- Simplify series resistors:

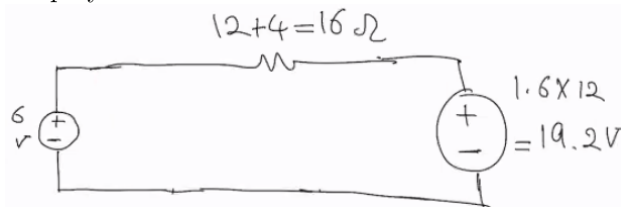

- Now we can use KVL on this loop to find the current in this circuit and get the power
- If we have a voltage source in parallel with a resistor, the value of the resistance does not affect the voltage distributed to the rest of the circuit, so it doesn't impact the rest of the circuit
  - Since the resistor has no affect on the rest of the circuit, we can remove it altogether (open the circuit)
- If we have a current source in series with a resistor, the value of the resistance does not affect the current distributed to the rest of the circuit, so it has no impact either
  - Since it has no affect, we can remove it (short the circuit)